



SCHOOL OF ELECTRICAL ENGINEERING

LAB MANUAL / RECORD

On

EEE 4028

VLSI DESIGN

LABORATORY

(Fall Semester -2017-18)

Name: **Divyang Thakkar**

Register Number: **15BEE0174**

LAB SLOT: L23+L24

This work is submitted in partial fulfilment of the requirement of the award of the degree of Bachelor of Technology in EEE.

Internal Examiner

External Examiner

Objectives:

- To provide students with the background needed to design, develop, and test digital arithmetic circuits using IEEE standard Verilog HDL.
- To provide an understanding complex arithmetic circuit design principle and its architecture design.


Outcomes:

- After completion of this course the students will be familiar with design and implementation of Digital Arithmetic building blocks using Verilog HDL and Xilinx FPGA Design Flow.





EXPT 2: 4-BIT CARRY LOOK AHEAD ADDER







Objective: To design, implement and test a 4-bit CARRY LOOK AHEAD ADDER circuit.

Circuit Diagram:

 

Logic Gate Diagram:

    

      

DESIGN CODE:

```
module CLA(  
    input [3:0] a,  
    input [3:0] b,  
    input cin,  
    output [3:0] s,  
    output cout  
);  
  
wire [4:0] c;  
wire [3:0] p,g;  
assign c[0]=cin;  
assign p= a^b;  
assign g= a&b;  
assign s= p^c[3:0];  
assign c[1] = (p[0]&c[0])|g[0];  
assign c[2] = (p[1]&p[0]&c[0])|(p[1]&g[0])|g[1];  
assign c[3] = (p[1]&p[0]&p[2]&c[0])|(p[1]&p[2]&g[0])|(p[2]&g[1])|g[2];  
assign c[4] = (p[3]&p[1]&p[2]&p[0]&c[0])|(p[1]&p[2]&p[3]&g[0])|(p[2]&p[3]&g[1])|(p[3]&g[2]|g[3]);  
assign cout = c[4];  
endmodule
```

TEST BENCH CODE:

```
module CLA_4bit;

    // Inputs

    reg [3:0] a;

    reg [3:0] b;

    reg cin;

    // Outputs

    wire [3:0] s;

    wire cout;

    reg [4:0] check;

    CLA uut (

        .a(a),

        .b(b),

        .cin(cin),

        .s(s),

        .cout(cout)

    );

    // Initialize Inputs

    initial repeat(20) begin

        a=$random;

        b=$random;

        cin=$random;

        check = a+b+cin;

        // Wait 100 ns for global reset to finish

        #10 $display($time,"%d+%d+%d=%d(%d)",a,b,cin,{cout,s},check);

    end

endmodule
```

RESULT:

Successfully designed, implemented and tested CARRY LOOK AHEAD ADDER circuit using Xilinx ISE tool.

Device utilization summary:

Selected Device: 3s500efg320-4

Number of Slices: 4 out of 4656 0%

Number of 4 input LUTs: 8 out of 9312 0%

Number of IOs: 14

Number of bonded IOBs: 14 out of 232 6%

Partition Resource Summary:

No Partitions were found in this design

Timing Summary:

Speed Grade: -4


Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 9.838ns

OUTPUT:

 

10 4+ 1+1= 6(6)
 20 3+13+1=17(17)
 30 5+ 2+1= 8(8)
 40 13+ 6+1=20(20)
 50 13+12+1=26(26)
 60 6+ 5+0=11(11)
 70 5+ 7+0=12(12)
 80 15+ 2+0=17(17)
 90 8+ 5+0=13(13)
 100 13+13+1=27(27)
 110 3+10+0=13(13)
 120 0+10+1=11(11)
 130 6+ 3+1=10(10)
 140 3+11+1=15(15)
 150 2+14+1=17(17)
 160 15+ 3+0=18(18)
 170 10+12+0=22(22)
 180 10+ 1+0=11(11)
 190 8+ 9+1=18(18)
 200 6+ 6+0=12(12)

Lab Work: Carry Look Ahead Adder

3/8/17.

Verilog

Test

Fixture

(Exp-2)

```
module CLA_4bit;
```

```
reg [3:0] a;
```

```
reg [3:0] b;
```

```
wire [3:0] s;
```

```
wire cout;
```

```
reg [4:0] check;
```

```
CLA uut (
```

```
    .a(a)
```

```
    .b(b)
```

```
    .cin(cin)
```

```
    .s(s)
```

```
    .cout(cout)
```

```
);
```

```
initial repeat(20) begin
```

```
    a = $random;
```

```
    b = $random;
```

```
    cin = $random;
```

```
    check = a + b + cin;
```

```
#10 $display($time, "%d + %d + %d = %d(%d)",
```

```
    a, b, cin, {cout, s}, check);
```

```
end
```

```
endmodule;
```